



BERZIET UNIVERSITY

Faculty of Engineering and Technology  
Electrical and Computer Engineering Department

**ANALOG ELECTRONICS**  
**ENEE2360**  
**PSpice project part2**

---

Student's name: Sara Issa

Student's ID: 1190673

Instructor's name: Dr. Naser Ismail

Section No. 2

Teacher assistant's name: Eng. Bilal Ismail

Date: 05.01.2021

# Abstract:

The aim of this project is to know how to use Pspice software to design and simulate the room thermostat to keep the room temperature between two threshold temperatures TH (15 °C) and TL (13 °C) that mean the heater turns off when the temperature goes over TH and turns on when the temperature goes below TL. Then, the comparison between the resulting values from the calculation process and the resulting values from the curves to find out the error percentage.

## Table of Contents:

1. Procedure and Discussion .....	3
1.1. The Bipolar Junction Transistor .....	3
1.2. The Operational Amplifier .....	3
1.1. The calculation before designing the circuit .....	4
1.3. The calculation after designing the circuit .....	8
2. Conclusion .....	9
3. References .....	10

# 1. Procedure and Discussion:

To complete the design of the room thermostat shown in Figure NO.1 to keep the room temperature between two threshold temperatures TH (15 °C) and TL (13 °C):

**NOTE:** The heater turns off when the temperature goes over TH and turns on when the temperature goes below TL.

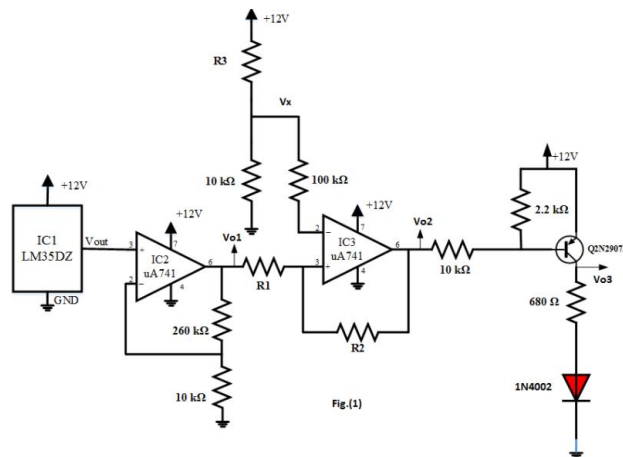


Figure NO.1: Circuit of the room thermostat

**The Bipolar Junction Transistor:** is a semiconductor device which can be used for switching or amplification. It's a three terminal device: Base, Emitter, and Collector. Also, there are two type of BJT: NPN type and PNP type as shown in Figure NO.2:

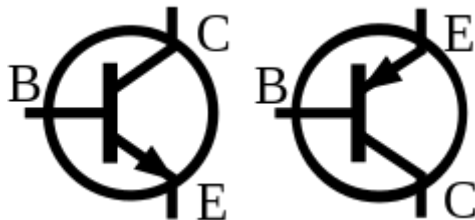


Figure NO.2: BJTs NPN and PNP schematic symbols [1]

**The Operational Amplifier:** is an integrated circuit that can amplify weak electric signals. An operational amplifier has two input pins and one output pin. Its basic role is to amplify and output the voltage difference between the two input pins as shown in Figure NO.3:

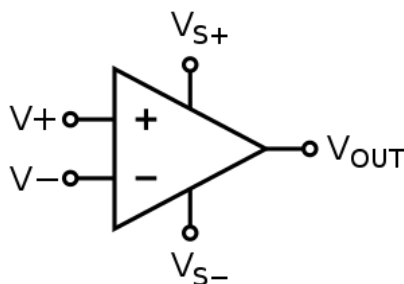


Figure NO.3: Circuit diagram symbol for an Operational amplifier [2]

### The calculation before designing the circuit (from the given values):

#### 1. Non inverting amplifier “Negative feedback”:

- **Case 1:** when  $T_L = 13^\circ\text{C}$ , then  $V = 10\text{m volt}/^\circ\text{C} * 13^\circ\text{C} = 0.13\text{ volt}$ :

$$V_{o1} = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_+ = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_{\text{out}} = 27 * 0.13 = 3.51\text{ volt}.$$

- **Case 2:** when  $T_H = 15^\circ\text{C}$ , then  $V = 10\text{m volt}/^\circ\text{C} * 15^\circ\text{C} = 0.15\text{ volt}$ :

$$V_{o1} = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_+ = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_{\text{out}} = 27 * 0.15 = 4.05\text{ volt}.$$

#### 2. Schmitt trigger (hysteresis) “Positive feedback”:

- No current pass in  $R_7 = 100\text{ k ohm}$ , because  $i_7 = i_- = 0\text{A}$ .
- $3.51\text{ volt} < V_x < 4.05\text{ volt}$ , so assume  $V_x = V_- = \frac{3.51 + 4.05}{2} = 3.78\text{ volt}$ .
- By voltage divider rule “to find the value of  $R_3$ ”:

$$V_- = V_x = 12 * \frac{10\text{ k ohm}}{R_3 + 10\text{ k ohm}} = \frac{120\text{ k ohm}}{R_3 + 10\text{ k ohm}} = 3.78\text{ volt}.$$

$$\therefore R_3 = 21746.03175\text{ ohm} = 21.75\text{ k ohm}.$$

- In schmitt trigger (hysteresis) “Positive feedback”  $V_o = \mp V_{\text{sat}}$ :

- I. Let  $V_{o2} = +V_{\text{sat}} = 11.6\text{ volt}$ , then  $V_d = V_+ - V_- > 0$ ,  $V_+ > V_- = V_x = 3.78\text{ volt}$ .

By superposition:

- A. Kill  $V_{o1}$ :

$$V_+ = \frac{R_1}{R_1 + R_2} * V_{o2} = \frac{R_1}{R_1 + R_2} * (+V_{\text{sat}}) = \frac{11.6 R_1}{R_1 + R_2}.$$

- B. Kill  $V_{o2}$ :

$$V_+ = \frac{R_2}{R_1 + R_2} * V_{o1} = \frac{3.51 R_2}{R_1 + R_2}.$$

$$\therefore \text{So } V_+ = \frac{11.6 R_1 + 3.51 R_2}{R_1 + R_2} > 3.78 \dots (1)$$

- II. Let  $V_{o2} = -V_{\text{sat}} = 0.4\text{ volt}$ , then  $V_d = V_+ - V_- < 0$ ,  $V_+ < V_- = V_x = 3.78\text{ volt}$ .

By superposition:

- A. Kill  $V_{o1}$ :

$$V_+ = \frac{R_1}{R_1 + R_2} * V_{o2} = \frac{R_1}{R_1 + R_2} * (-V_{\text{sat}}) = \frac{0.4 R_1}{R_1 + R_2}.$$

- B. Kill  $V_{o2}$ :

$$V_+ = \frac{R_2}{R_1 + R_2} * V_{o1} = \frac{4.05 R_2}{R_1 + R_2}.$$

$$\therefore \text{So } V_+ = \frac{0.4 R_1 + 4.05 R_2}{R_1 + R_2} < 3.78 \dots (2)$$

By subtracting equation number 2 from equation number 1:

$$\frac{11.2 R_1}{R_1 + R_2} - \frac{0.54 R_2}{R_1 + R_2} = 0 \rightarrow \left(\frac{11.2 R_1}{R_1 + R_2} = \frac{0.54 R_2}{R_1 + R_2}\right) * R_1 + R_2, \text{ then } \frac{R_2}{R_1} = 20.74074074$$

Assume  $R_1 = 100\text{ k ohm}$ , then  $R_2 = 2074.074074\text{ k ohm}$ .

- When  $V_{o1} \downarrow$ ,  $V_{o1} > 3.51\text{ volt} \rightarrow V_{o2} = +V_{\text{sat}}$ . But when  $V_{o1} < 3.51\text{ volt} \rightarrow V_{o2} = -V_{\text{sat}}$ .
- When  $V_{o1} \uparrow$ ,  $V_{o1} < 4.05\text{ volt} \rightarrow V_{o2} = -V_{\text{sat}}$ . But when  $V_{o1} > 4.05\text{ volt} \rightarrow V_{o2} = +V_{\text{sat}}$ .

Using PSPICE ,determine  $V_x, V_{o1}, V_{o2}, V_{o3}$ , and the status of (the BJT and the diode) at  $T = 8^\circ\text{C}$  and  $T = 32^\circ\text{C}$  ( $V_{\text{out}} = 0.08\text{V}$  and  $V_{\text{out}} = 0.32\text{V}$ ):

**At  $T = 8^\circ\text{C}$  and  $V_{\text{out}} = 0.08\text{V}$ :**

$V_{o1} = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_+ = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_{\text{out}} = 27 * 0.08 = 2.16\text{ volt}$ . And  $V_{o2} = 387.06\text{ mV} = 0.38706\text{ V} \cong -V_{\text{sat}} = 0.4\text{ V}$ . Then, threshold temperature  $= 8^\circ\text{C} < T_L = 13^\circ\text{C}$ , so the heater turns on.

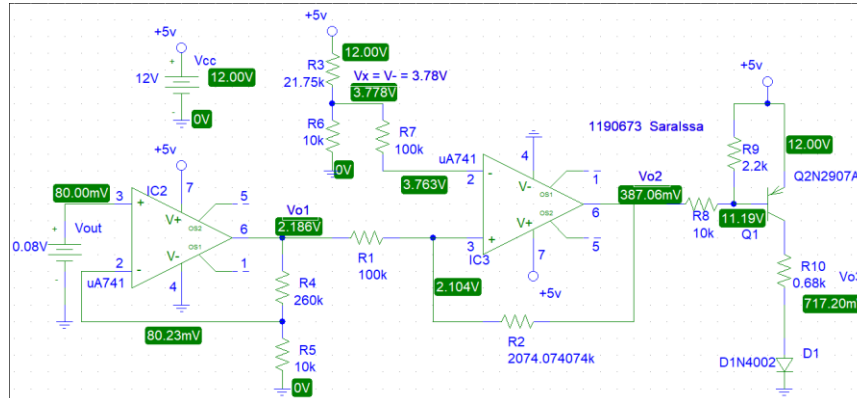


Figure NO.4: Circuit of the room temperature when threshold temperature  $8^\circ\text{C}$  in Pspice

**At  $T = 32^\circ\text{C}$  and  $V_{\text{out}} = 0.32\text{V}$ :**

$V_{o1} = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_+ = \left(1 + \frac{260\text{ k ohm}}{10\text{ k ohm}}\right) * V_{\text{out}} = 27 * 0.32 = 8.64\text{ volt}$ . And  $V_{o2} = 11.61\text{V} \cong +V_{\text{sat}} = 11.6\text{ V}$ . Then, threshold temperature  $= 32^\circ\text{C} > T_H = 15^\circ\text{C}$ , so the heater turns off.

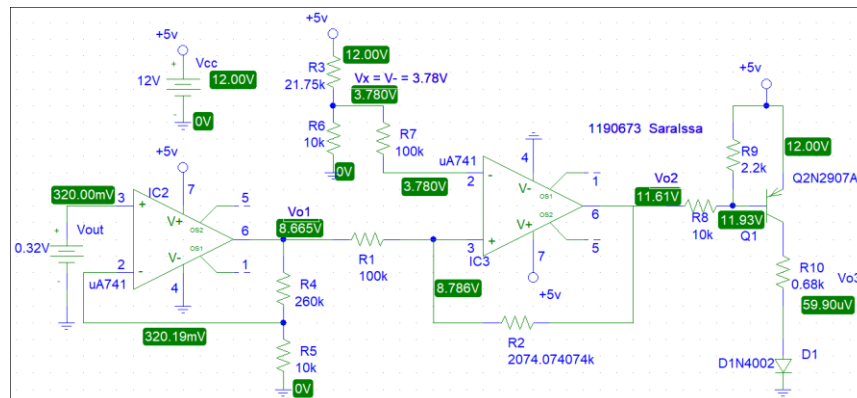


Figure NO.5: Circuit of the room temperature when threshold temperature  $32^\circ\text{C}$  in Pspice

**The Circuit of the room temperature between two threshold temperatures  $T_H$  ( $15^\circ\text{C}$ ) and  $T_L$  ( $13^\circ\text{C}$ ) in Pspice as shown in Figure NO.6:**

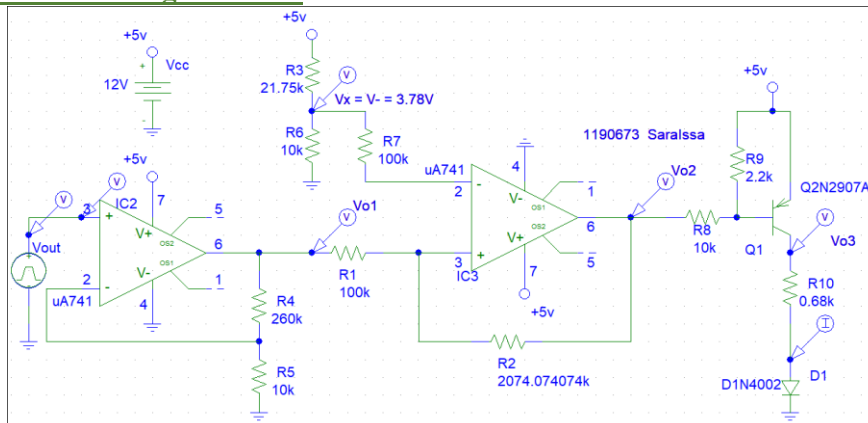


Figure NO.6: Circuit of the room temperature between two threshold temperatures  $T_H$  ( $15^\circ\text{C}$ ) and  $T_L$  ( $13^\circ\text{C}$ ) in Pspice

**The output of simulation of Vpulse when the temperature increases from 8 °C to 32 °C, that after set the values in Vpulse as shown in adjacent figure:**

The temperature increases from 8 °C to 32 °C.

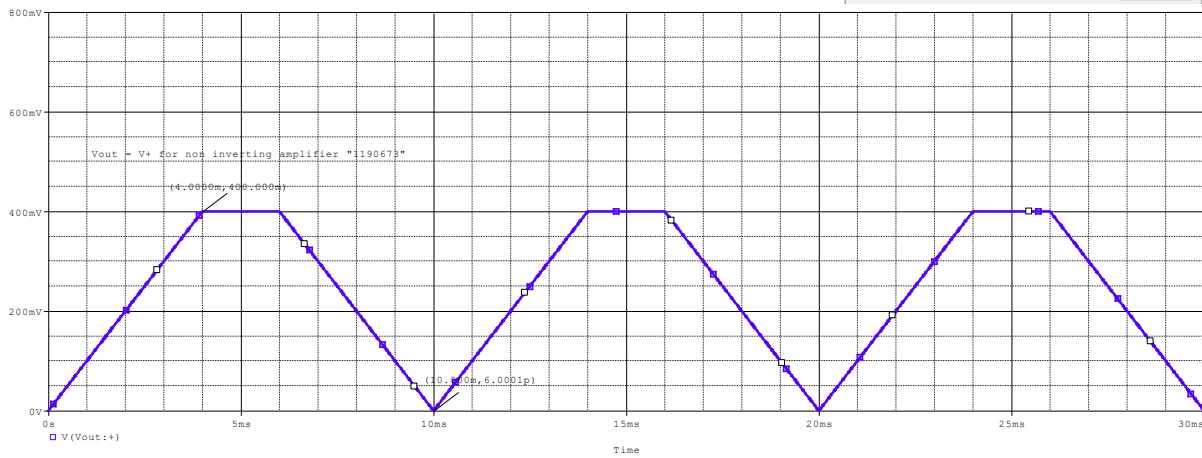
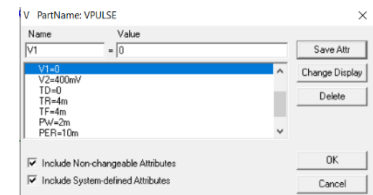


Figure NO.7: The output of simulation of Vpulse in Pspice

**Plot Vo1(t) from circuit Simulation:**

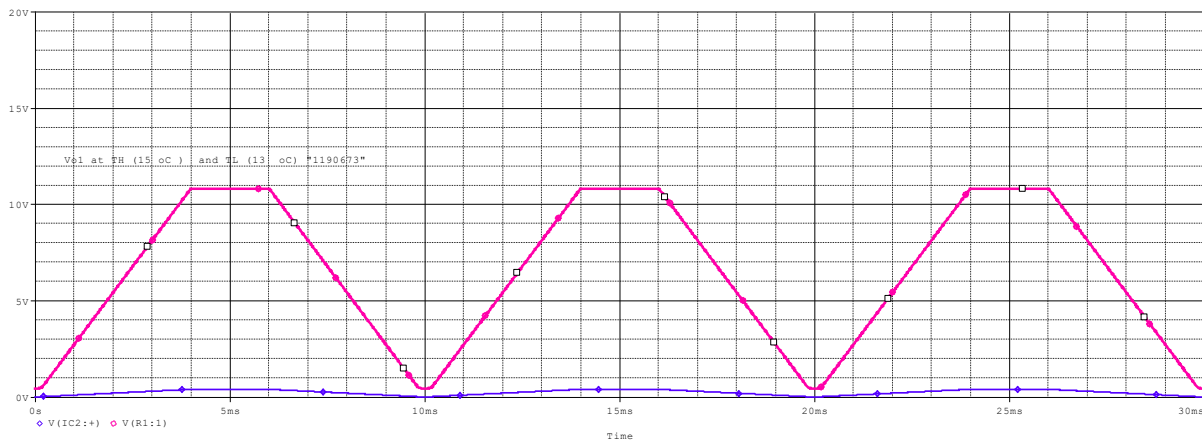


Figure NO.8: Vo1(t) from circuit Simulation in Pspice

**Plot Vx = V- for schmitt trigger (hysteresis) from circuit Simulation:**

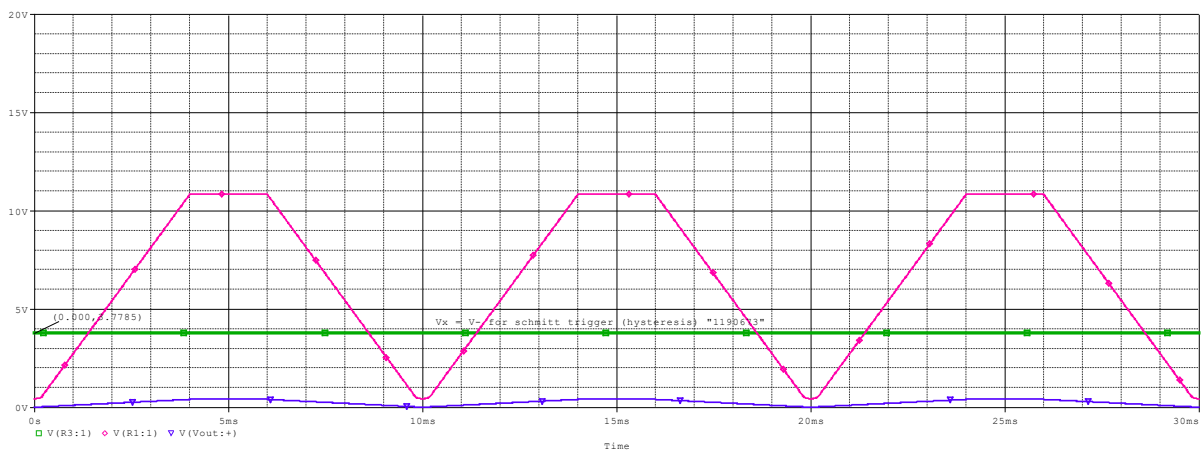


Figure NO.9: Vx = V- for schmitt trigger (hysteresis) in Pspice

### Plot $V_{o2}(t)$ from circuit Simulation:

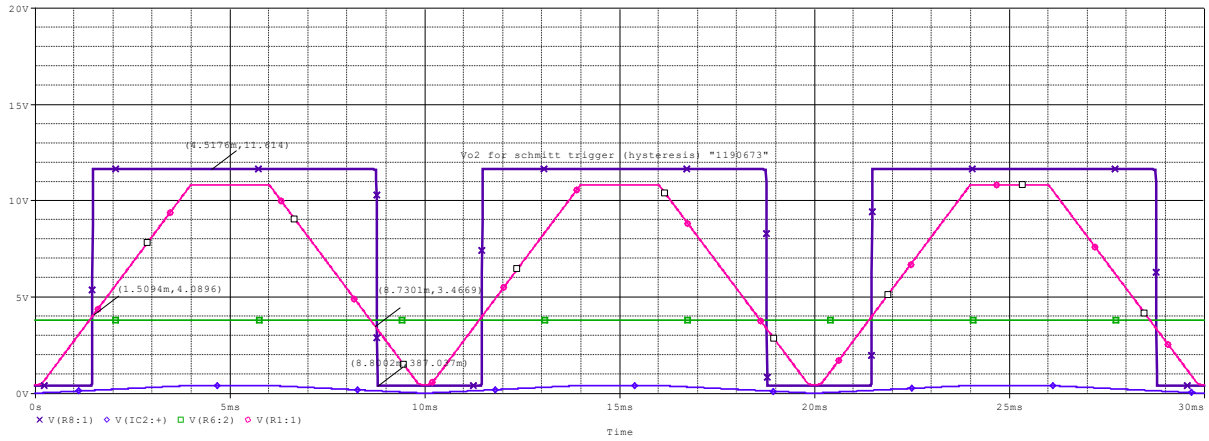


Figure NO.10:  $V_{o2}(t)$  from circuit Simulation in Pspice

### Plot $V_{o3}(t)$ from circuit Simulation:

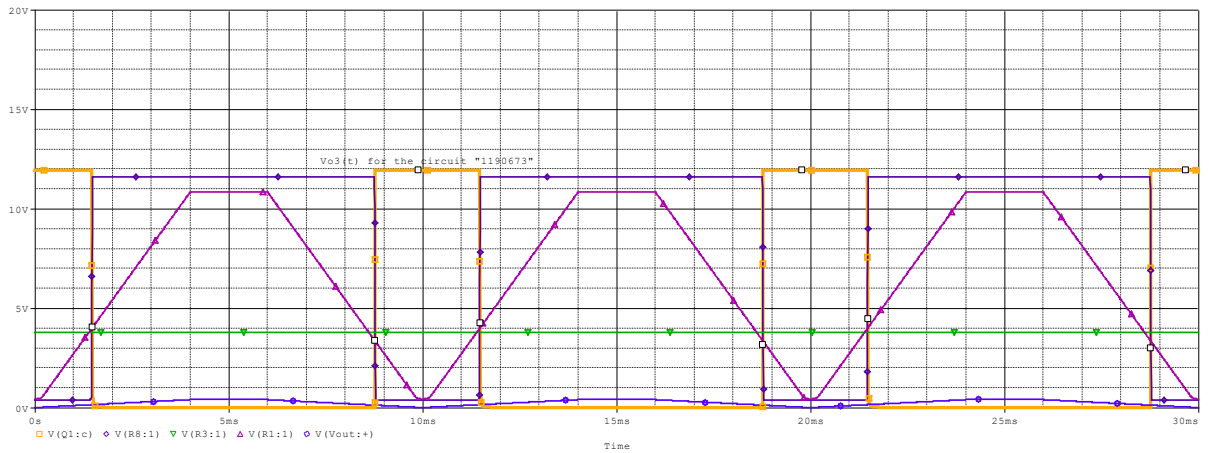


Figure NO.11:  $V_{o3}(t)$  from circuit Simulation in Pspice

### Plot $I_D$ from circuit Simulation:

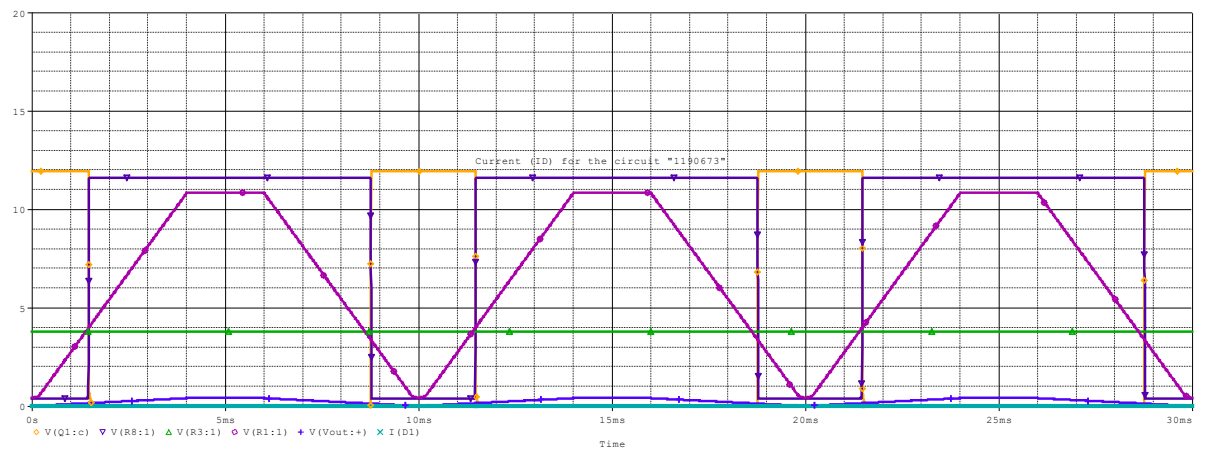


Figure NO.12:  $I_D$  from circuit Simulation in Pspice



The output of simulation of Vpulse when the temperature decreases from 32 °C to 8 °C, that after set the values in Vpulse as shown in adjacent figure:

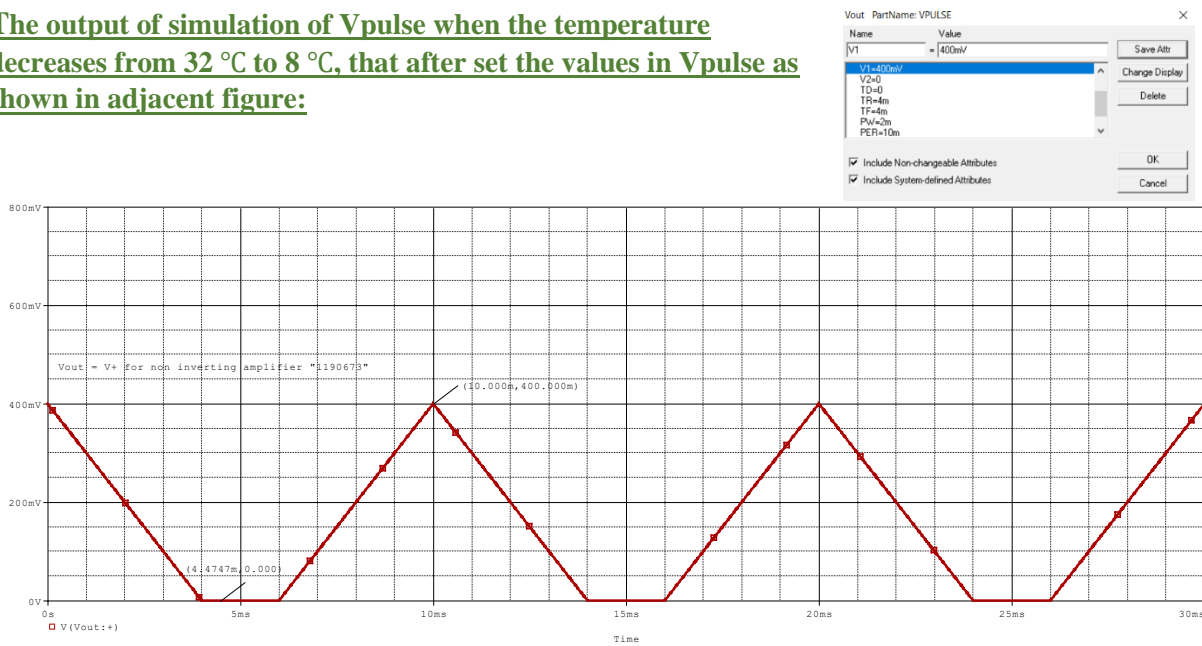


Figure NO.13: The output of simulation of Vpulse in Pspice

Plot  $V_x, V_{o1}, V_{o2}, V_{o3}$  from circuit Simulation as the temperature decreases from 32 °C to 8 °C:

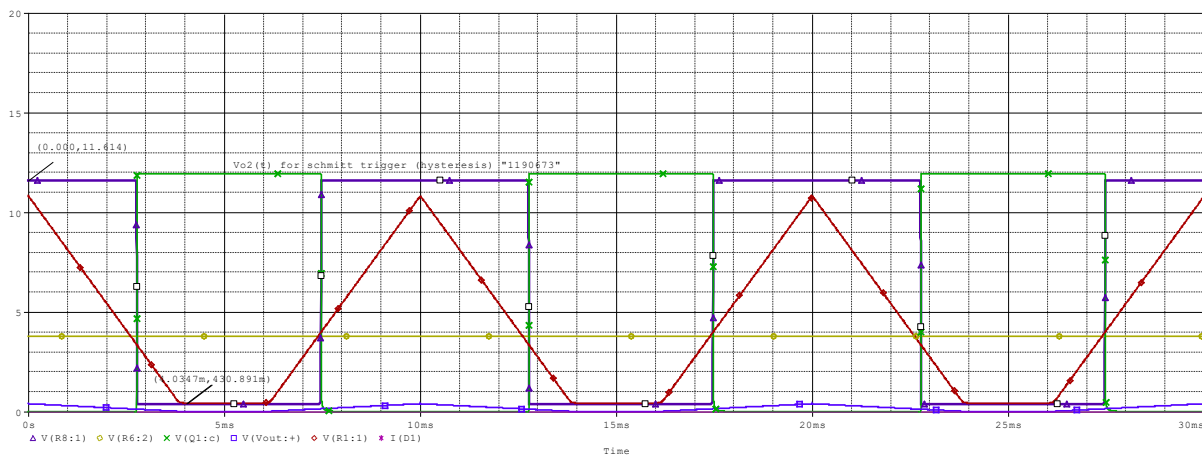


Figure NO.14: The output of plot  $V_x, V_{o1}, V_{o2}, V_{o3}$

The calculation after designing the circuit (from the curves):

From the previous curves:

- At temp =  $T_H = 15^\circ\text{C}$ , then  $V_{o1} = 4.0896\text{ volt}$ .
- At temp =  $T_L = 13^\circ\text{C}$ , then  $V_{o1} = 3.4669\text{ volt}$ .
- When  $V_{o2} = +V_{sat} = 11.614\text{ volt}$ .
- When  $V_{o2} = -V_{sat} = 387.037\text{ mV} = 0.387037\text{ volt}$ .
- $V_x = V_{\text{-for schmitt trigger (hysteresis)}} = 3.7785\text{ volt}$ .

**2. Conclusion:** The heater turns off when the temperature goes over TH (temp > 15°C), this means that no current passes through the diode (therefore, if the place of the diode was a led, it will be turn off), ID (when temp = 32 °C) = 16.60pA  $\cong$  0 A, as shown in Figure NO.15:

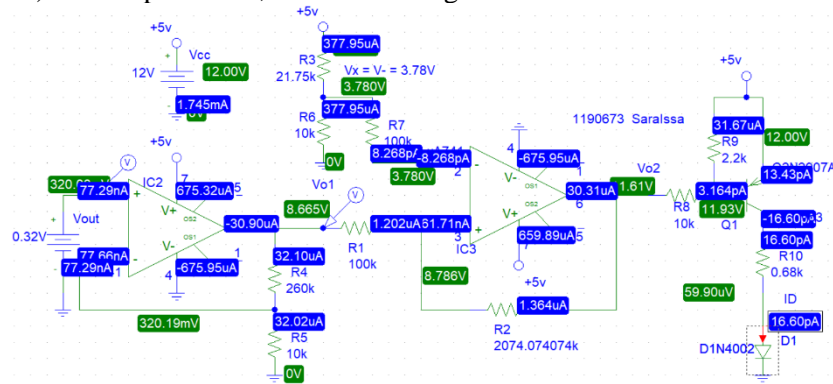


Figure NO.15: The heater turns off when the temperature goes over TH

And the heater turns on when the temperature goes below TL (temp < 13°C), this means that current passes through the diode (therefore, if the place of the diode was a led, it will be turn on), ID (when temp = 8 °C) = 16.49 mA, as shown in Figure NO.16:

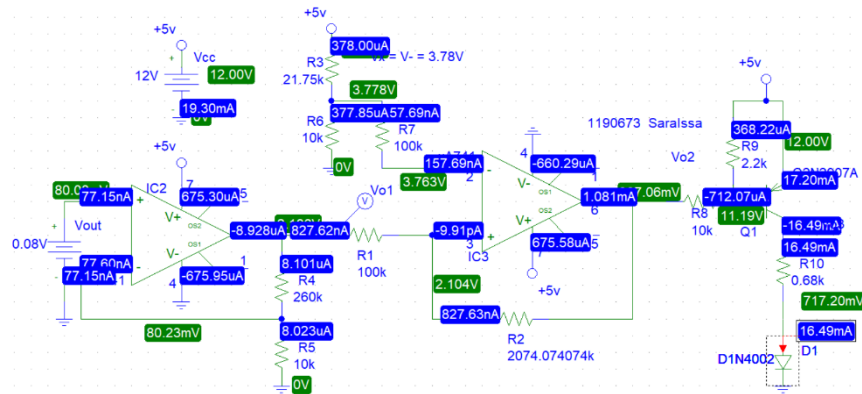


Figure NO.16: The heater turns on when the temperature goes below TL

**Note:** BJT transistor controls whether the heater turns on or off, so either both of them is On or Off.

Comparison of the results between simulated values of  $V_x$ ,  $V_{o1}$  and  $V_{o2}$  to hand calculations, as shown in Table NO.1:

Name of voltage	simulated values	Hand calculations values
$V_x$	3.7785 volt	3.78 volt
$V_{o1}$ at 13 °C	3.4669 volt	3.51 volt
$V_{o1}$ at 15 °C	4.0896 volt	4.05 volt
$V_{o2} = +V_{sat}$	11.614 volt	11.6 volt
$V_{o2} = -V_{sat}$	0.387037 volt	0.4 volt

From the previous table, it was found that the values of  $V_x$ ,  $V_{o1}$  and  $V_{o2}$  were very similar. Error percentage in the room temperature between two threshold temperatures TH (15 °C) and TL (13 °C):

Error percentage =  $[V_{o2}(\text{simulation}) - V_{o2}(\text{given})] / V_{o2}(\text{given}) * 100\% = (11.614 - 11.6) / 11.6 * 100\% = 0.120689\%$  very small percentage, and error percentage  $\ll 5\%$  so it's accepted.

### 3. References:

1. "What is an Operational Amplifier?," 30 Dec 2021. [Online]. Available: <https://www.ablic.com/en/semicon/products/analog/opamp/intro/>.
2. "lecture notes," 20 NOV 2021. [Online]. Available: [https://drive.google.com/drive/folders/1BMOtKtk\\_tsWvnqLaALTTrSv28DYf2cHz](https://drive.google.com/drive/folders/1BMOtKtk_tsWvnqLaALTTrSv28DYf2cHz)
3. "Bipolar junction transistor," 29 Dec 2021. [Online]. Available: [https://en.wikipedia.org/wiki/Bipolar\\_junction\\_transistor](https://en.wikipedia.org/wiki/Bipolar_junction_transistor).
4. "Circuit diagram symbol for an Operational amplifier," 30 Dec 2021. [Online]. Available: [https://www.google.com/url?sa=i&url=https%3A%2F%2Fwww.wikiwand.com%2Fen%2FOperational\\_amplifier&psig=AOvVaw1Jk-waHfXm-l8LL9vibobE&ust=1641551531546000&source=images&cd=vfe&ved=0CAsQjRxqFwoTCLCmipb2nPUCFQAAAAAdAAAAABAD](https://www.google.com/url?sa=i&url=https%3A%2F%2Fwww.wikiwand.com%2Fen%2FOperational_amplifier&psig=AOvVaw1Jk-waHfXm-l8LL9vibobE&ust=1641551531546000&source=images&cd=vfe&ved=0CAsQjRxqFwoTCLCmipb2nPUCFQAAAAAdAAAAABAD).